

HACETTEPE UNIVERSITY
DEPARTMENT OF COMPUTER ENGINEERING
BBM231 LOGIC DESIGN

Homework 2 (For all sections)

Assigned : 5.11.2018


Due : 12.11.2018

Hand in your homework solutions in class.

QUESTIONS:


Q1. Simplify the following Boolean functions using four-variable maps:

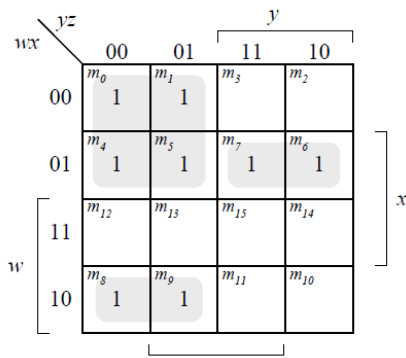a) $F(w, x, y, z) = \sum(0, 1, 4, 5, 6, 7, 8, 9)$



(c) $F = w'y' + wx'y' + w'xy$

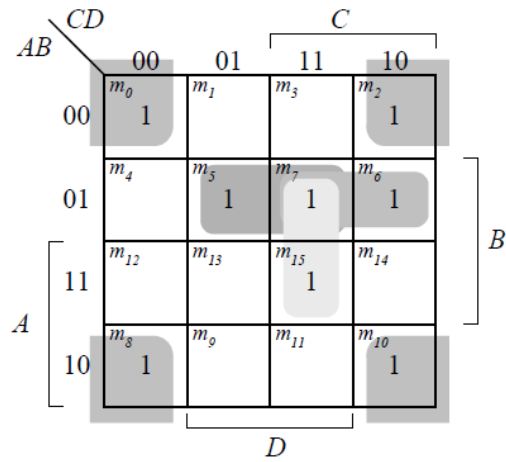
b) $F(A, B, C, D) = A'B'C'D' + A'CD' + AB'D' + ABCD + A'BD$



(c) $F = B'D' + BCD + A'BD + A'BC$


Q2. Find all the prime implicants for the Boolean functions and determine which are essential:

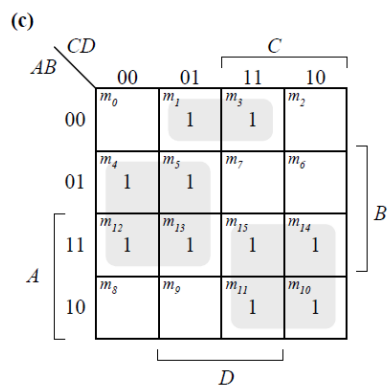a) $F(A, B, C, D) = \sum(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$



Essential: $BC', AC, A'B'D$
 $F = BC' + AC + A'B'D$

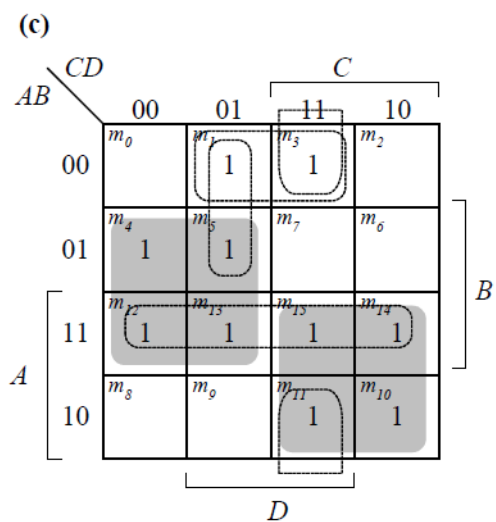b) $F(w, x, y, z) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$



Essential: BC', AC

Non-essential: $AB, A'B'D, B'CD, A'C'D$

$F = BC' + AC + A'B'D$

Q3. Given $h = f \oplus g$,

$$f(w,x,y,z) = \sum(2,3,5,6,7,12,13,15),$$


$$g(w,x,y,z) = \sum(1,3,4,5,6,8,11,12,14,15),$$

find the minimal expression for $h(w,x,y,z)$ and draw its circuit using minimum number of two-input-gates. You can use AND, OR, NOT, XOR gates with two-inputs.

	w	x	y	z	f	g	h
0	0	0	0	0	0	0	0
1	0	0	0	1	0	1	1
2	0	0	1	0	1	0	1
3	0	0	1	1	1	1	0
4	0	1	0	0	0	1	1
5	0	1	0	1	1	1	0
6	0	1	1	0	1	1	0
7	0	1	1	1	1	0	1
8	1	0	0	0	0	1	1
9	1	0	0	1	0	0	0
10	1	0	1	0	0	0	0
11	1	0	1	1	0	1	1
12	1	1	0	0	1	1	0
13	1	1	0	1	1	0	1
14	1	1	1	0	0	1	1
15	1	1	1	1	1	1	0


wx \ yz	00	01	11	10
00		1		1
01	1		1	
11		1		1
10	1		1	

$$h = w \oplus x \oplus y \oplus z$$

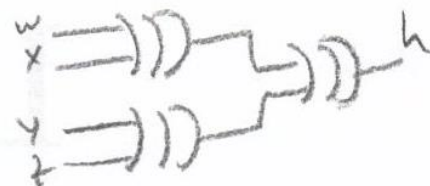

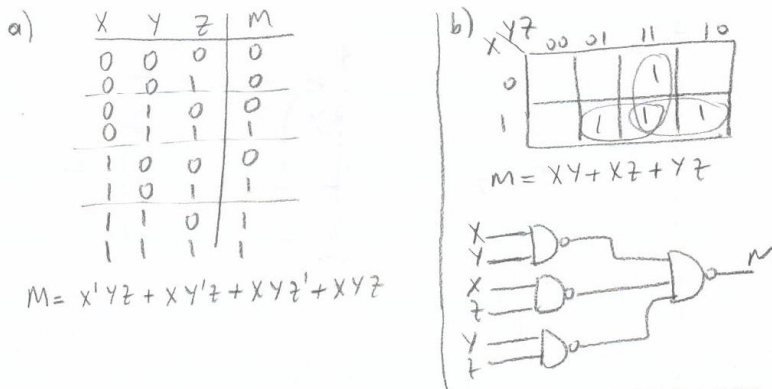Q4. A majority function has an output value of one if there are more 1s than 0s on its inputs.

- Express three input majority function in sum of minterms form after filling the truth table.
- Implement the **optimized circuit** with only NAND gates.




Q5. Implement the following Boolean function F , together with the don't-care conditions d , using no more than two NOR Gates.

$$F(A, B, C, D) = \sum(2, 4, 6, 10, 12)$$

$$d(A, B, C, D) = \sum(0, 8, 9, 13)$$

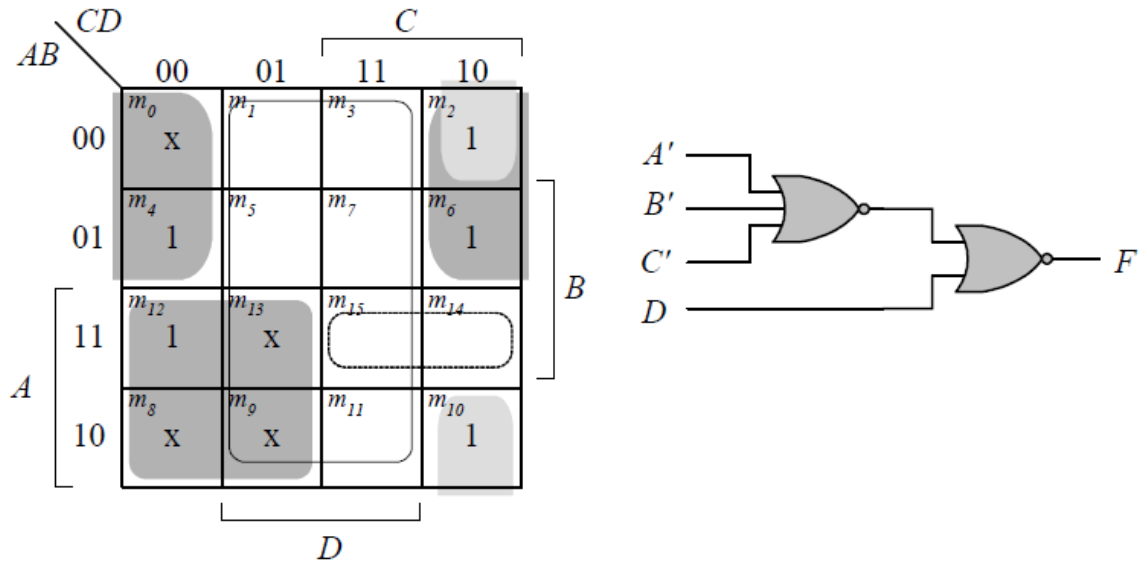Assume that both the normal and complement inputs are available.



$$F = AC' + A'D' + B'CD'$$

$$F' = D + ABC$$

$$F = [D + ABC]' = [D + (A' + B' + C')]'$$