

Name-Last name :

Student No :

Section :

FİZ 138 PHYSICS II

MIDTERM EXAM I


March 28, 2017

13:00 – 14:30 (90 min)

1	
2	
3	
4	
5	


Questions

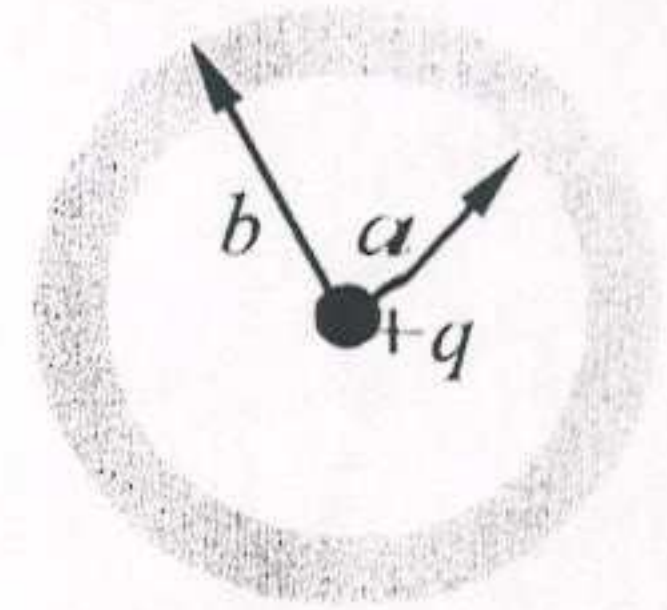1. Figure shows a nonconducting spherical shell, of inner radius a and outer radius b , has a positive volume charge density $\rho = A/r$ (within its thickness), where A is a constant and r is the distance from the center of the shell. In addition, a positive charge q is located at the center. What value should A have if the electric field in the shell ($a \leq r \leq b$) is to be uniform?




2. In a region where the electric potential is given by $V(x,y,z) = 2x^2 + yz$, find the electric field at the point with coordinates $x = 2$, $y = 1$, and $z = 2$. Everything is in SI units.
3. A spherical capacitor has radii a and b . What is the radius r for which the energy stored within, i.e., the spherical shell from radius a to radius r , is one third ($1/3$) of the total energy stored in the capacitor?

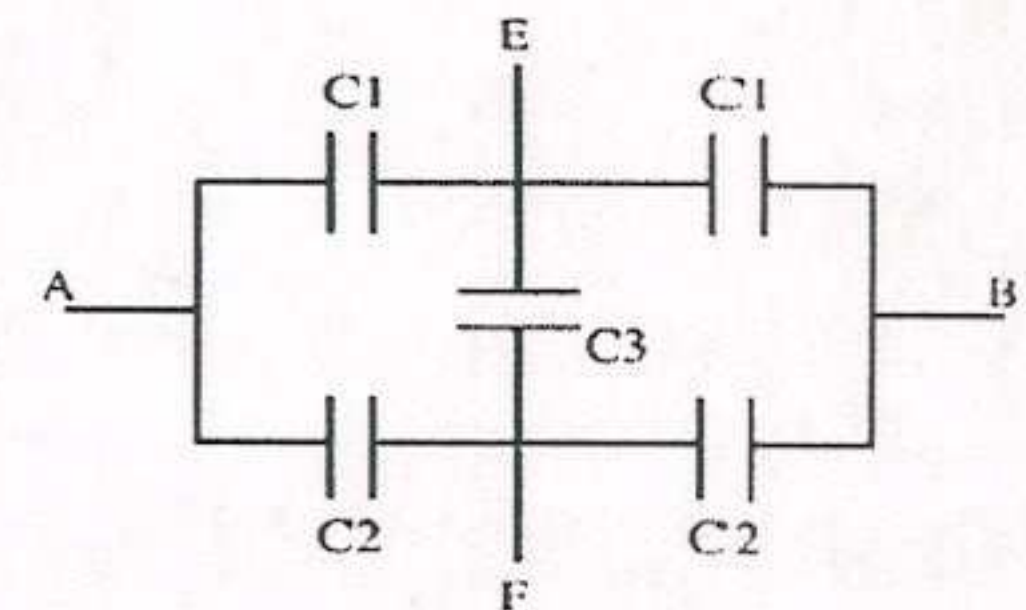4. Calculate the equivalent capacitance (in terms of C_1 , C_2 and C_3)
- C_{AB} between the points A and B,
 - C_{EF} between the points E and F.



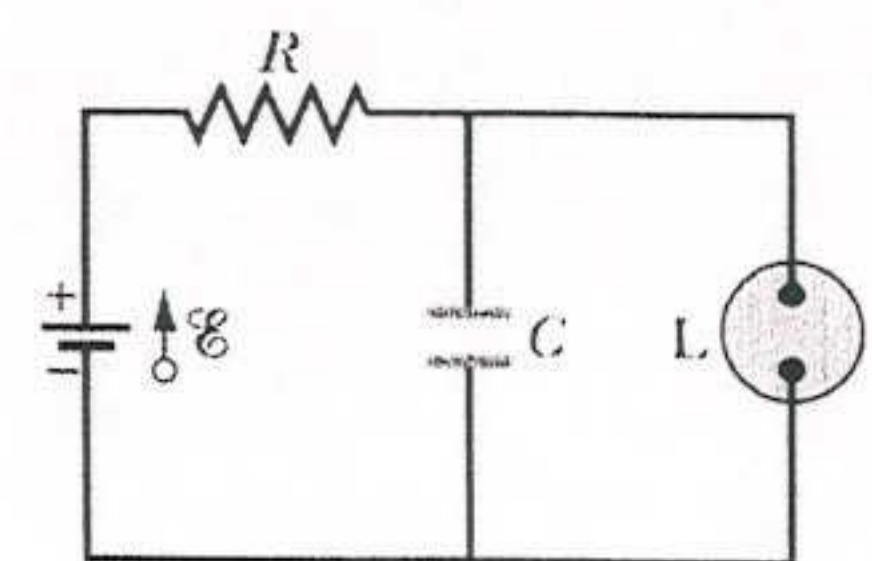5. The fluorescent lamp L only functions when the potential difference across it reaches V_L — below that value, no current passes through it; then the capacitor discharges completely through the lamp and the lamp flashes briefly.



- With C , ϵ (ideal *emf* device) and V_L given, calculate the necessary R in order to achieve n flashes per second from the lamp.
- If the circuit is turned on at $t = 0$, plot the voltage across the lamp's terminals with respect to time.

Charge on a charging capacitor: $q(t) = \epsilon C [1 - \exp(-t/RC)]$

Charge on a discharging capacitor: $q(t) = q_0 \exp(-t/RC)$

1) $\epsilon_0 E(a) 4\pi a^2 = q$ (1) ← central charge
 $\epsilon_0 E(r) 4\pi r^2 = q + \int_a^r dr' 4\pi r'^2 \frac{A}{r'} = q + 4\pi A \frac{1}{2} (r^2 - a^2)$ (2) ← charge in the shell (a to r)

$E = \text{uniform} \rightarrow E(a) = E(r) = E$

$$E = \frac{1}{4\pi\epsilon_0} \frac{q}{a^2} = \frac{1}{4\pi\epsilon_0} \frac{1}{r^2} [q + 2\pi A(r^2 - a^2)]$$

$$\rightarrow \frac{qr^2}{a^2} = q + 2\pi A(r^2 - a^2)$$

$$q\left(\frac{r^2}{a^2} - 1\right) = 2\pi A(r^2 - a^2)$$

$$q \frac{(r^2 - a^2)}{a^2} \frac{1}{2\pi(r^2 - a^2)} = A \Rightarrow A = \frac{q}{2\pi a^2}$$

2) $E_i = -\frac{dV}{dx_i} \rightarrow \begin{cases} E_x = -4x \\ E_y = -z \\ E_z = -y \end{cases} \begin{cases} \vec{E}(x, y, z) = -4x\hat{i} - z\hat{j} - y\hat{k} \\ \vec{E}(2, 1, 2) = (-8\hat{i} - 2\hat{j} - \hat{k}) \text{ N/C} \end{cases}$

3) 1st Way

$$u = \frac{1}{2} \epsilon_0 E^2 \text{ : Energy Density}$$

$$E(r) = \frac{Q}{4\pi\epsilon_0 r^2} \rightarrow u = \frac{1}{2} \epsilon_0 \frac{Q^2}{16\pi^2 \epsilon_0^2 r^4}$$

$$dU = u \cdot dV = \frac{1}{2} \frac{Q^2}{16\pi^2 \epsilon_0 r^4} 4\pi r^2 dr$$

$$dU = \frac{Q^2}{8\pi\epsilon_0 r^2} dr$$

$$\frac{1}{3} = \frac{\int_a^r \frac{Q^2}{8\pi\epsilon_0 r'^2} dr'}{\int_a^b \frac{Q^2}{8\pi\epsilon_0 r'^2} dr'} = \frac{-\left[\frac{1}{r} - \frac{1}{a}\right]}{-\left[\frac{1}{b} - \frac{1}{a}\right]} = \frac{a-r}{dr} \cdot \frac{ab}{a-b}$$

2nd Way

$$U = \frac{1}{2} QV$$

$$E(r) 4\pi r^2 \epsilon_0 = Q \rightarrow E(r) = \frac{Q}{4\pi\epsilon_0 r^2}$$

$$V(r) = -\int_a^r E(r') dr' = -\frac{Q}{4\pi\epsilon_0} \int_a^r \frac{dr'}{r'^2}$$


$$= \frac{Q}{4\pi\epsilon_0} \left[\frac{1}{r} - \frac{1}{a} \right] = \frac{Q}{4\pi\epsilon_0} \frac{(a-r)}{ar}$$

$$\frac{1}{3} = \frac{\frac{1}{2} Q V(r)}{\frac{1}{2} Q V(b)} = \frac{V(r)}{V(b)} = \frac{(a-r)}{ar} \cdot \frac{ab}{(a-b)}$$

$$\frac{1}{3} = \frac{(a-r)b}{(a-b)r} \rightarrow \begin{aligned} 3ab - 3br &= ar - br \\ 3ab &= r(a-b+3b) \end{aligned}$$

$$r = \frac{3ab}{a+2b}$$

Wheatstone Bridge Revisited

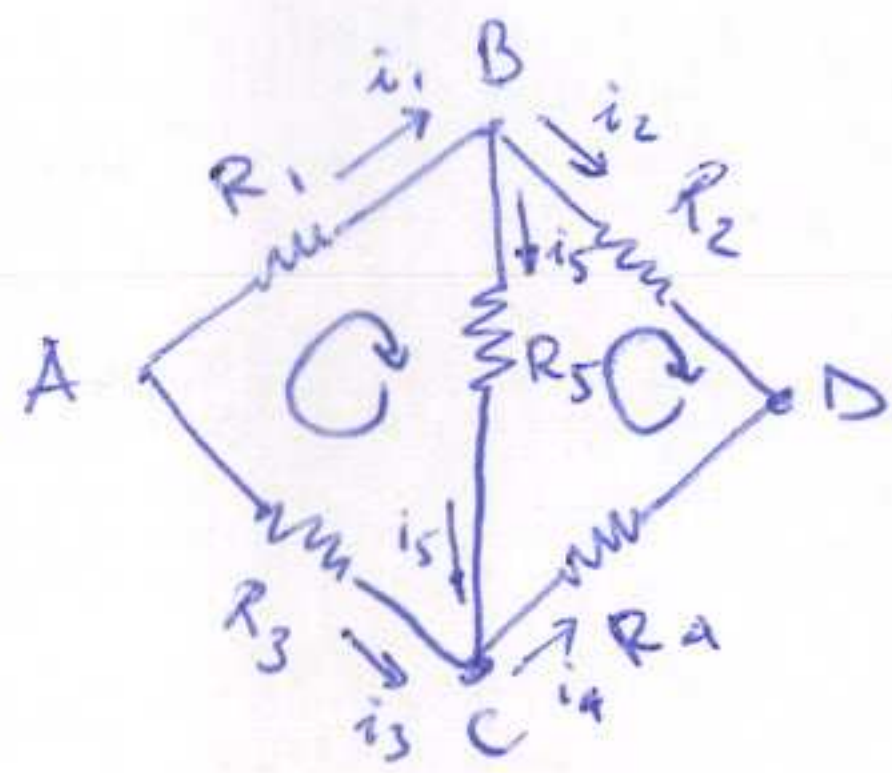

5 unknowns = i_1, i_2, i_3, i_4, i_5

$$B: i_1 - i_2 - i_5 = 0$$

$$C: i_3 + i_5 - i_4 = 0$$

$$ABC: -i_1 R_1 - i_5 R_5 + i_3 R_3 = 0$$

$$BDC: -i_2 R_2 + i_4 R_4 + i_5 R_5 = 0$$

4 equations

(ABCD is just

ABC + BDC, so nothing new)

5 unknowns - 4 equations = Not sufficient

Let's assume $i_5 = 0$. Then: $B: i_1 - i_2 = 0 \rightarrow i_1 = i_2 \equiv i_A$


$$C: i_3 - i_4 = 0 \rightarrow i_3 = i_4 \equiv i_B$$

$$ABC: -i_A R_1 + i_B R_3 = 0 \rightarrow i_A R_1 = i_B R_3$$


$$BDC: -i_A R_2 + i_B R_4 = 0 \rightarrow i_A R_2 = i_B R_4 \rightarrow \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\Rightarrow \boxed{i_5 = 0 \iff \frac{R_1}{R_2} = \frac{R_3}{R_4}}$$

4) a) AB (Wheatstone Bridge)

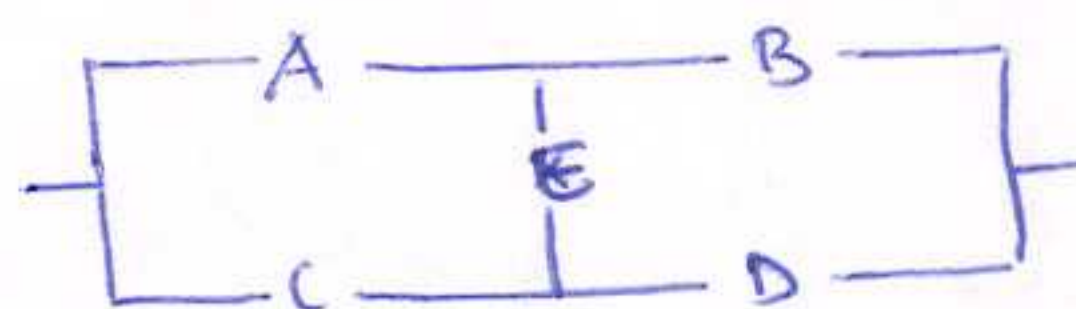
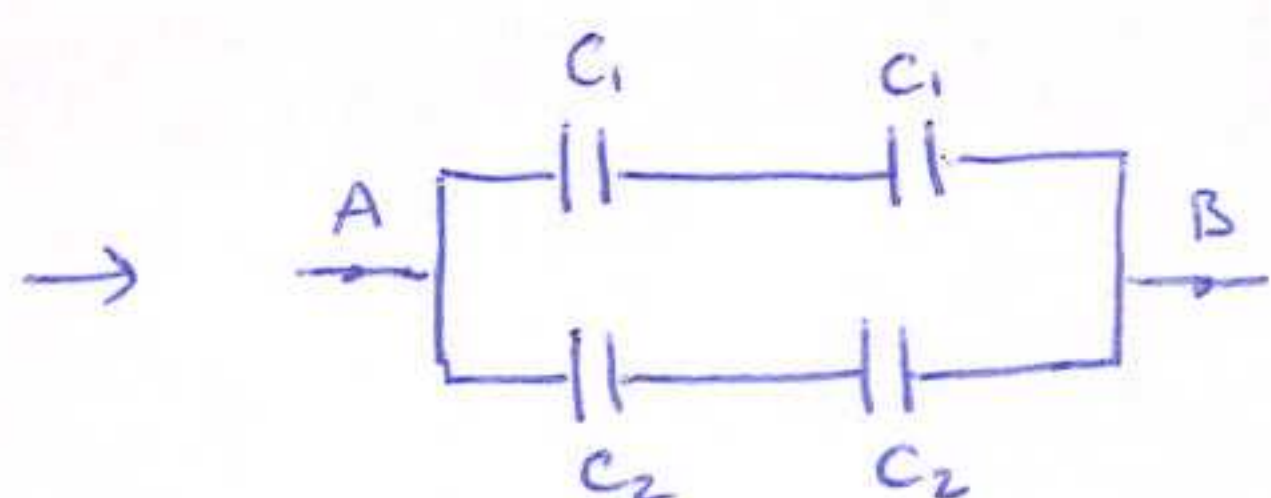
$$\frac{V_A}{V_B} = \frac{V_C}{V_D} \Rightarrow i_E = 0$$




$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_1} \right)^{-1} + \left(\frac{1}{C_2} + \frac{1}{C_2} \right)^{-1}$$

$$= \frac{C_1}{2} + \frac{C_2}{2} = \frac{C_1 + C_2}{2}$$

$$\frac{C_1}{C_1} = \frac{C_2}{C_2} \rightarrow i_3 = 0$$

b) EF

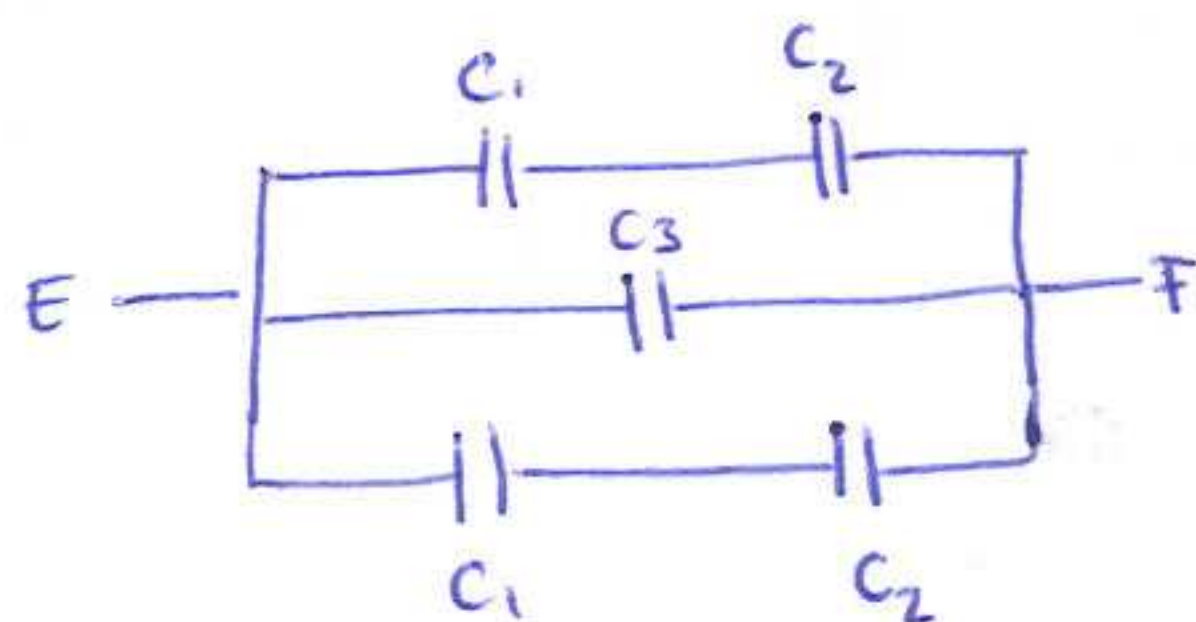

$$C_{eq} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} + C_3 + \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1}$$

$$= 2 \frac{C_1 C_2}{C_1 + C_2} + C_3$$

$$= \frac{2 C_1 C_2 + C_1 C_3 + C_2 C_3}{C_1 + C_2}$$

$$5) a) V = \frac{Q}{C} \rightarrow V(t) = \frac{E}{n} [1 - \exp(-t/nRC)]$$

$$V = V_L \iff t = \frac{1}{n} \Rightarrow V_L = E [1 - \exp(-\frac{1}{nRC})]$$

$$1 - \frac{V_L}{E} = \exp(-\frac{1}{nRC})$$

$$\ln(1 - \frac{V_L}{E}) = -\frac{1}{nRC}$$

$$R = -\frac{1}{nC} \frac{1}{\ln(1 - \frac{V_L}{E})} = -\frac{1}{nC} \frac{1}{\ln(\frac{E - V_L}{E})} = \frac{1}{nC \ln(\frac{E}{E - V_L})}$$

b)

